

Electronic Devices and Analog Circuits

■ Lecture 7


- ▼ Inductors
- ▼ DC motors
- ▼ Inductive power generation
- ▼ Diodes for rectification
- ▼ DC regulator circuits

Objectives of this Lecture

- Introduce inductor elements
- Describe inductance, and how it is used to create motors and generators
- Cover the basics regarding DC regulators and rectification
- Describe a DC-DC conversion circuit for use in Lab 2

Inductors

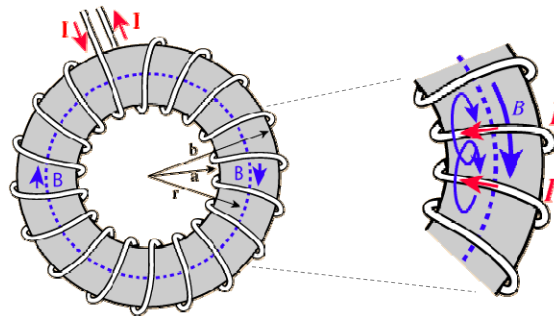- Inductor elements are created for use in filter circuits and for energy storage
- Often formed around materials with high permeability, μ , so that the flux lines are well contained




© Larry Pileggi, 2/1/2016

Slide 3

Inductors

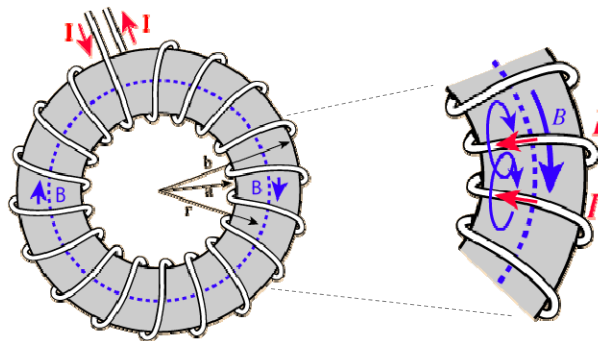- When we make inductors we often try to contain the magnetic fields by wrapping wires around a magnetic core
- A core is also used to precisely specify the number of loops
 - ▼ Example: Toroidal inductor where overall inductance is increased by the number of loops that are coupled





© Larry Pileggi, 2/1/2016

Slide 4

Toroidal Inductor

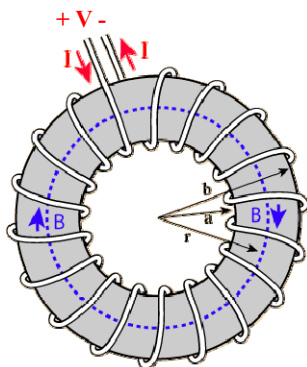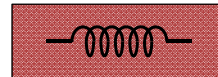- Represented as a lumped circuit element if flux is well contained



- From Maxwell: Flux Density

Permeability is measure of material's ability to support the formation of a magnetic field within itself. The degree of magnetization that a material obtains in response to an applied magnetic field [Henrys/meter]

$$B(t) = \frac{\mu \cdot N \cdot i(t)}{l(t)}$$

Number of turns

Length around core

Flux

- Flux through each turn (loop) is the integral of the flux density through the cross section of the core

$$\phi(t) = \int B \cdot dA = A \cdot B(t)$$

- Total flux is then:


$$\lambda(t) = N \cdot \phi(t) = N \cdot A \cdot B(t) \quad \text{Webers [Wb]}$$

$$B(t) = \frac{\mu \cdot N \cdot i(t)}{l}$$

$$\therefore \lambda(t) = \frac{\mu \cdot N^2 \cdot A}{l} \cdot i(t)$$

$$\lambda(t) = L \cdot i(t)$$
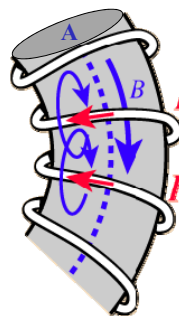
$$\therefore L = \frac{\mu \cdot N^2 \cdot A}{l} \quad \text{Wb/A [H]}$$



Inductor Equation


- Results in the simple expression for voltage and current relationship for a **linear time-invariant** inductor

$$L = \frac{\mu \cdot N^2 \cdot A}{l} \quad \text{Wb/A [H]}$$

$$\lambda(t) = L \cdot i(t)$$

$$v(t) = \frac{d\lambda(t)}{dt} = \frac{d[L \cdot i(t)]}{dt} = L \frac{di(t)}{dt}$$


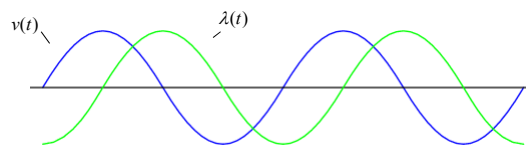
- For a sine wave voltage there is a phase shift with respect to the magnetic flux (hence the current)



Stored Energy



- Ignoring coil resistance, core loss and inter-turn capacitance for our linear time invariant toroidal inductor:

$$E = \frac{L \cdot i(t)^2}{2}$$

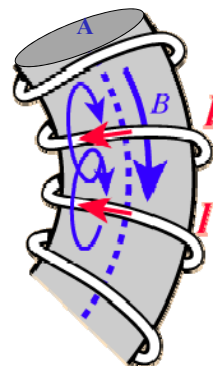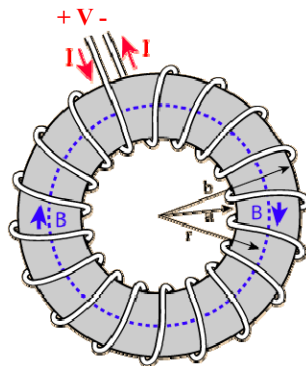

Inductance and Electric Motors and Generators

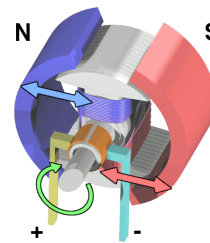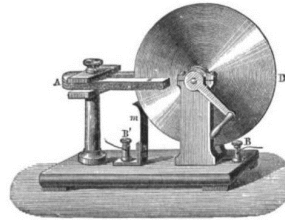
- Faraday showed that a force is produced on a current by a magnetic field
 - ▼ Faraday disk converts electrical energy into mechanical energy
 - ▼ Two interacting magnetic fields - one stationary, and another attached to a part that can move
- Modern DC motors and generators are based on the same principals



Fundamentals of a DC Motor


- Insert a current-carrying loop between two fixed magnets
- Connect the loop to a pivot point along its axis

Fixed magnets form the stator

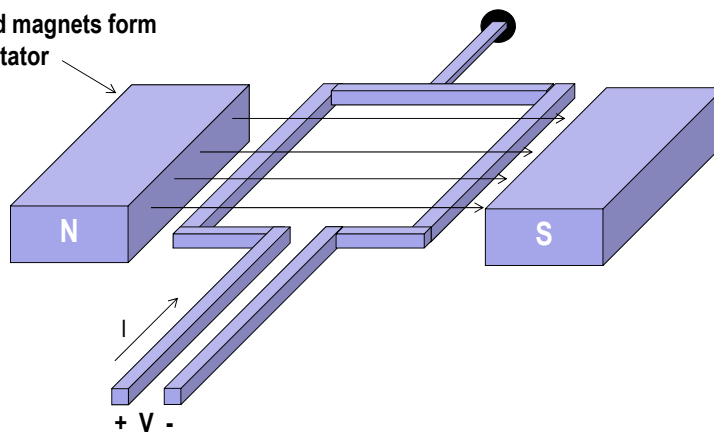

Fundamentals of a DC Motor

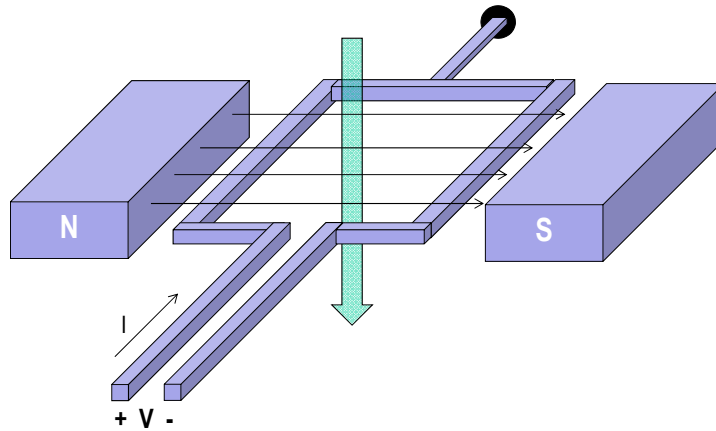- Rotor loop establishes a magnetic field direction due to DC current flow direction




© Larry Pileggi, 2/1/2016

Slide 11

Torque

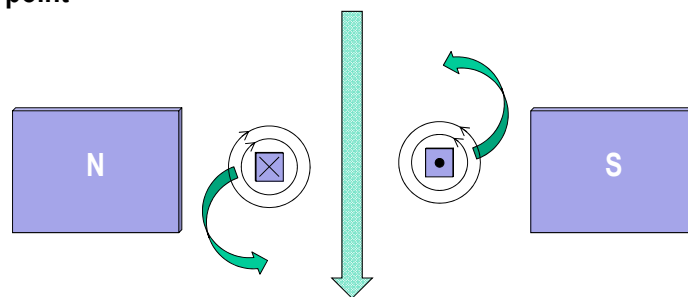- The magnetic field applies a torque to both sides of the metal loop
- The combined torque causes the loop to rotate about its pivot point




© Larry Pileggi, 2/1/2016

Slide 12


Torque

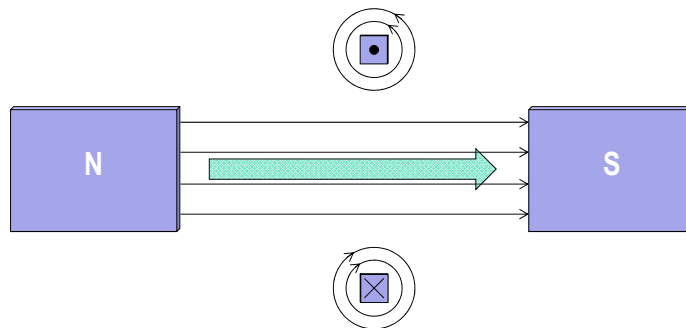- There is no torque at the neutral plane point, but inertia keeps the loop rotating



Rotation

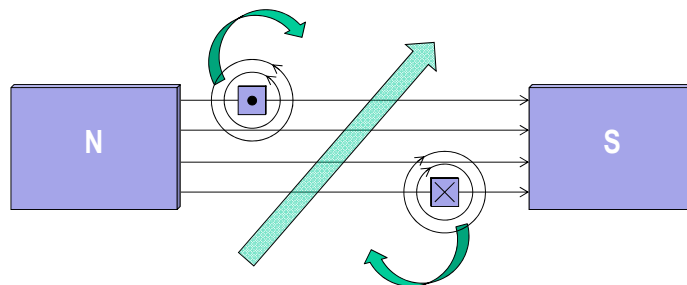
- If the currents remained in the same direction, the fields would now oppose this direction of rotation



- And an oscillating motion would be produced for the loop about its pivot axis


Brushes and Commutators

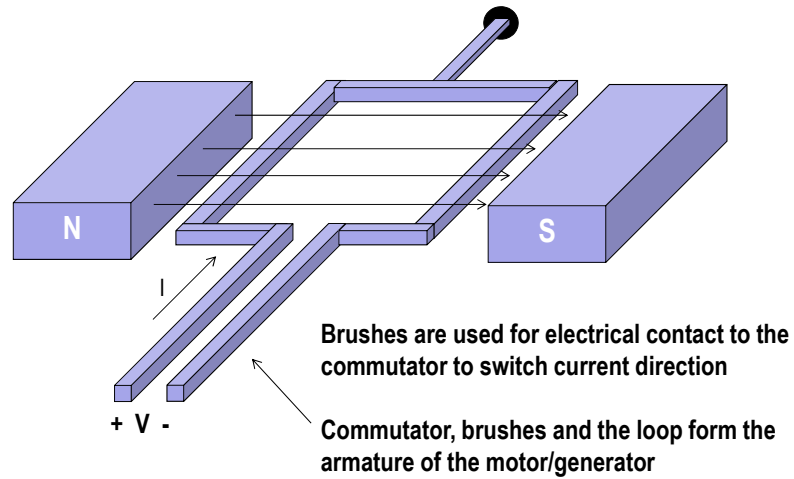- But instead, a commutator switches the direction of current when the loop passes through the neutral plane




dc Motor

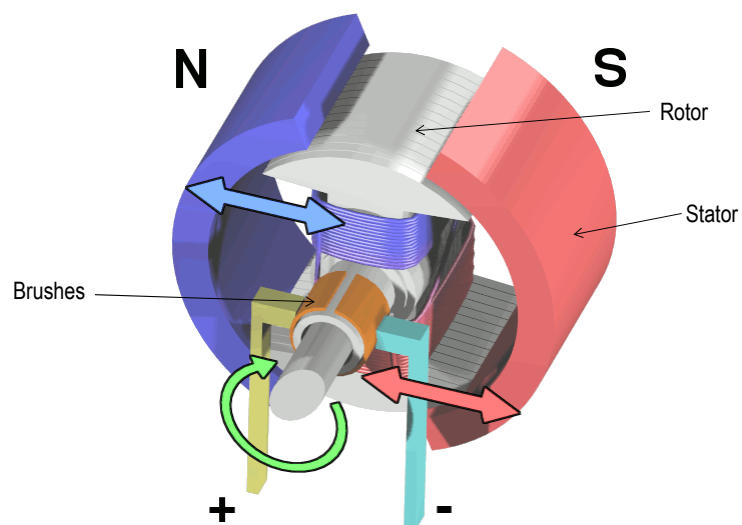- Rotor can generate more flux coupling with wound wire



Brushless dc Motors and Generators

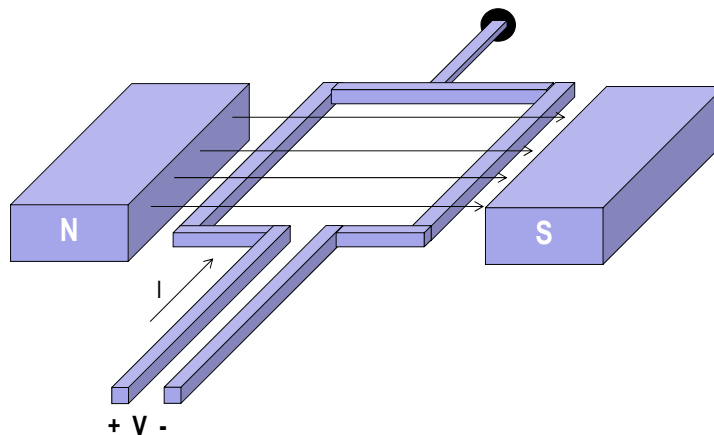- Brushes wear out, and can slow down the rotor assembly
- Inexpensive silicon chips and power transistors have enabled switching the current direction to be done electronically



© Larry Pileggi, 2/1/2016

Slide 17

Brushless dc Motors and Generators

- Can put the fixed magnets on the stator, or put them on the rotor and switch the stator electromagnetically
- Apply a dc voltage to a dc motor to form a current in the loop that causes the axis to spin
 - ▼ Moves a wheel, or a propeller, etc.
- Or, turn a crank to spin the loop and generate a voltage at the voltage leads
 - ▼ Is the voltage AC or DC?
 - ▼ Does it have a commutator or is it brushless?

© Larry Pileggi, 2/1/2016

Slide 18


Brushless dc Motors and Generators

- Depending on the switching method used by the controller, the current will be some time-varying (ac) signal
 - ▼ The frequency of this current signal will be related to the RPMs of the motor




Lab 2: Hand Cranked Cellphone Charger

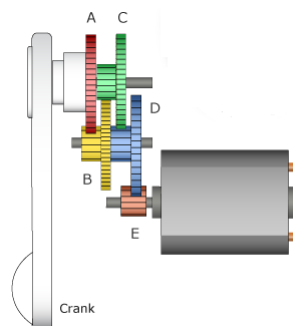- You will use a DC motor with a built-in gearbox
- Turning the crank through the gearbox will generate a time varying output voltage/current
- The voltage polarity will depend on which way we spin the rotor
- Use a full wave rectifier to extract the DC component for either polarity



Full-Wave Rectifier

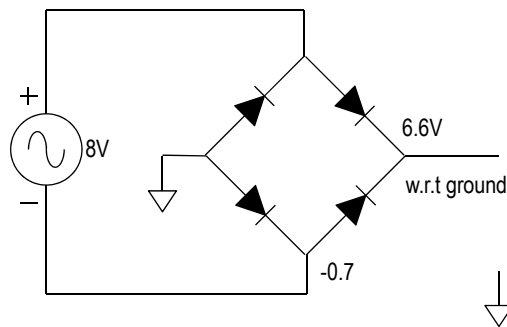- Full-wave rectifiers are most commonly used to generate dc voltages from ac power outlets
- Extracts the dc component from a positive or negative voltage signal




EXERCISE:

Confirm that the output voltage is the same w.r.t. ground for an input voltage of -8V


Full-Wave Rectifier

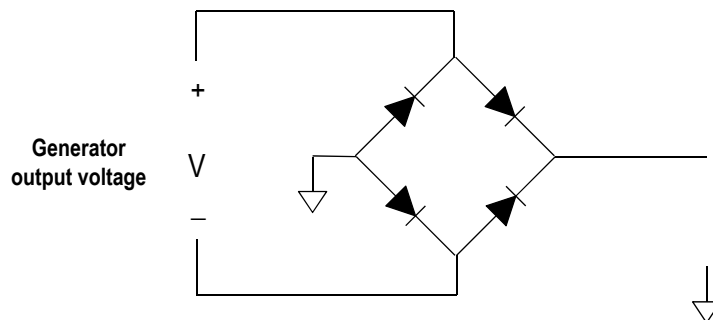- The diodes ensure that the time-varying positive or negative voltage from the generator produces a positive dc output



Diode Models

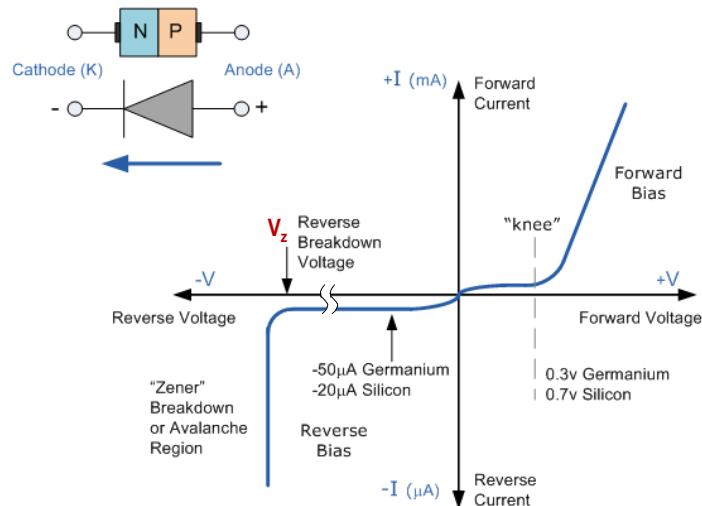- Diode reverse characteristic can be utilized as well




© Larry Pileggi, 2/1/2016

Slide 23

Full-Wave Rectifier

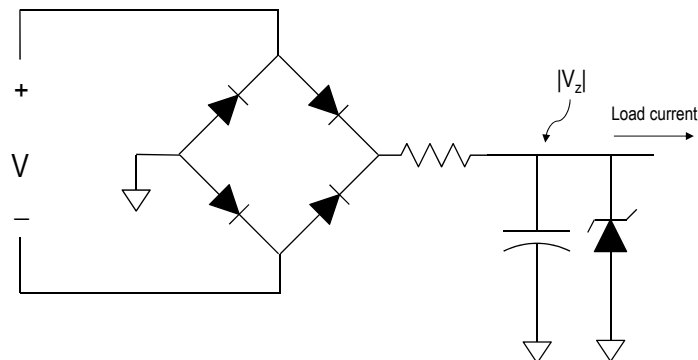- Use Zener diode to clamp the dc to a fixed value
- RC is used to smooth out the ripple
- The resistor also limits the current into the Zener diode, but thereby limits the maximum possible load current





© Larry Pileggi, 2/1/2016

Slide 24

Regulator Efficiency

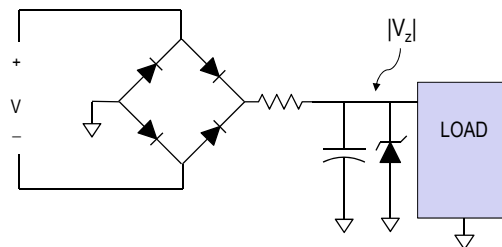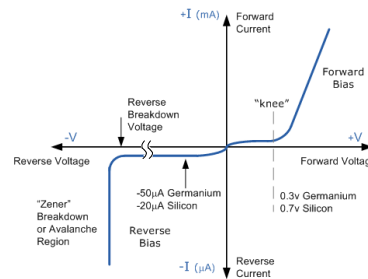- Load current will vary, but *near maximum* power is burned even for minimum loading condition




© Larry Pileggi, 2/1/2016

Slide 25

More Efficient Regulator

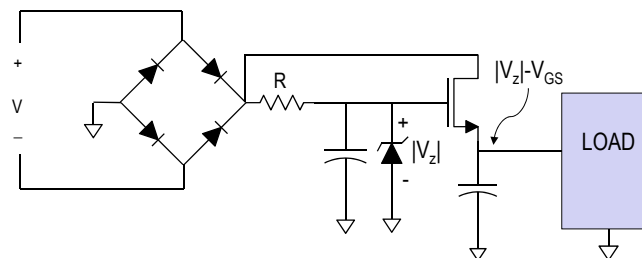- We can add a transistor to improve the efficiency
- **R can now be larger without limiting maximum loading current**
- But the DC voltage to the load now depends on the V_{GS} of the MOSFET




© Larry Pileggi, 2/1/2016

Slide 26

More Efficient Regulator

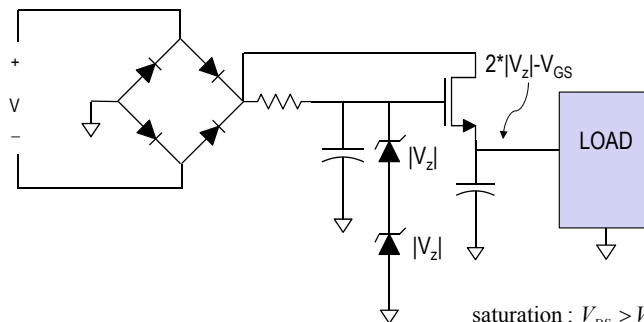- Would probably need more gate voltage for this to work
- But V_{GS} is still a function of the MOSFET (hence load) current
 - ▼ We don't want the voltage to change significantly with loading




saturation : $V_{DS} > V_{GS} - V_{TH}$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$

More Efficient Regulator

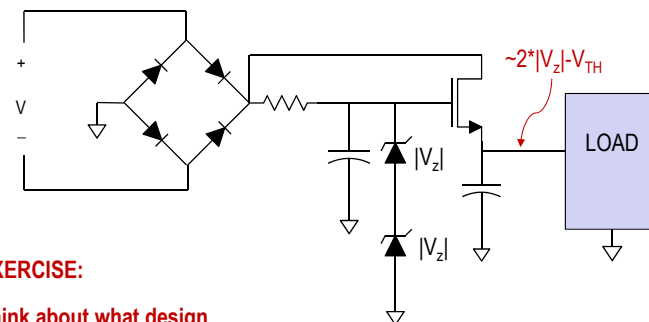- How could you select a MOSFET to make the load voltage no longer a function of V_{GS} , and approximately a function of V_{TH} ?



EXERCISE:


Think about what design parameters you would change, such as MOSFET size, to accomplish this

saturation : $V_{DS} > V_{GS} - V_{TH}$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$

More Efficient Regulator

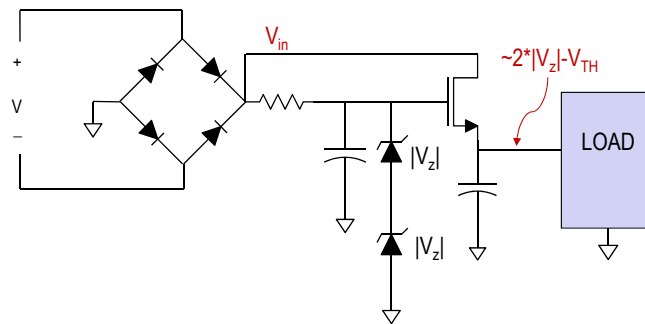
- But for large V_{in} the voltage drop across the MOSFET will dissipate a lot of unused power



- There are more efficient ways of doing DC-DC conversion

Low Loss Conversion

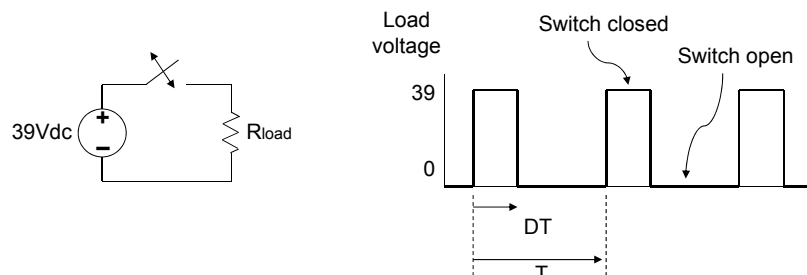
- Switch the large voltage into pulses of voltage
- Based on the duty cycle, D , the average voltage delivered to the load is reduced
 - ▼ Still need a low pass filter to convert AC pulses to DC value




If the duty cycle D of the switch is 0.33, then the average voltage to the load is 13Vdc

Buck Converter

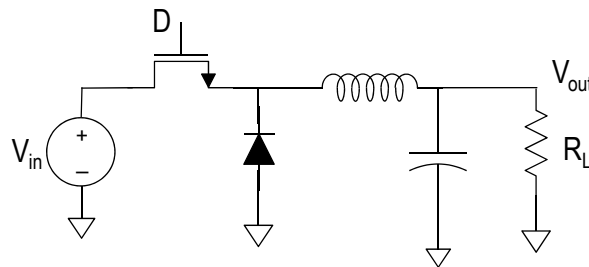- Buck converter – voltage step down, current step up
- An inductor and a capacitor form a lossless low-pass filter
- A MOSFET serves as the switch
- The diode serves as a current flow path when the switch is open



Buck Converter

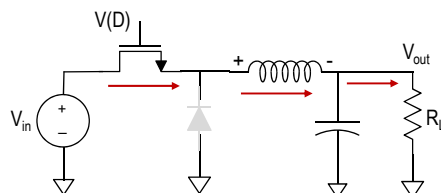


Switch closed:


$$v_L = V_{in} - V_{out} \quad \text{Diode is "off"}$$

$$\frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

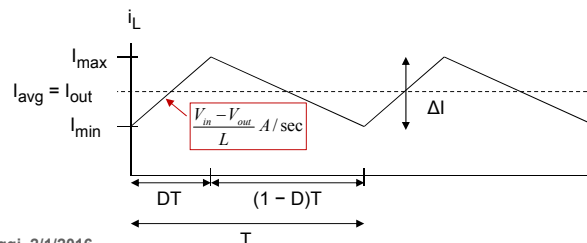- Inductor current increases which produces a voltage that opposes input voltage
- V_{out} is less than V_{in} based on drop across inductor
- D and T are chosen so that switch is opened while the inductor current is still changing, and energy is stored in the inductor of $0.5 \cdot L \cdot i^2$



Buck Converter

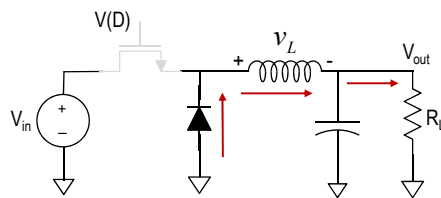


Switch open:

$$v_L = -V_{out}$$

$$\frac{di_L}{dt} = \frac{-V_{out}}{L}$$

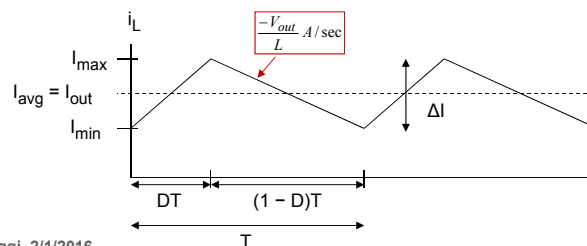- Inductor current decreases, which causes its voltage to change sign and now aid in the direction of supplying the load
- Inductor is delivering its stored energy to supply the load while switch is open
- Switch closes again while current is decreasing and inductor voltage is non-zero




© Larry Pileggi, 2/1/2016

Slide 33

Buck Converter

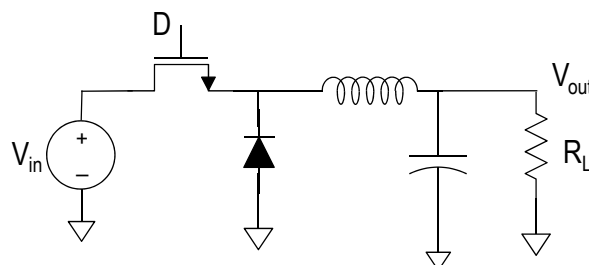- Capacitor helps to smooth out the voltage ripple
- LC filter effect will be covered in future lectures
- Time domain understanding of inductors should enable you to build a Buck Converter for your cellphone charger



© Larry Pileggi, 2/1/2016

Slide 34

Take Aways from this Video

- Understand the basics of forming an inductor element
- Have some idea of how you would calculate the inductance for a wound toroid
- Some basics regarding the operation of a DC motor
- A good start toward building your own Buck Converter in the lab