

# Electronic Devices and Analog Circuits

## ■ Lecture 3

- ▼ Diodes and LEDs
- ▼ Semiconductors
- ▼ MOSFETs

## ■ Reading:


- ▼ Sections 4.1-4.3
- ▼ Sections 6.1-6.3, 7.1-7.3

# Objectives of this Lecture

- Describe difference between linear and nonlinear circuit elements
- Introduce diodes and LEDs
  - ▼ Including models and how to use them
- Introduce MOSFETs
  - ▼ Just a start, since you'll see much more throughout the course
- Example diode problem

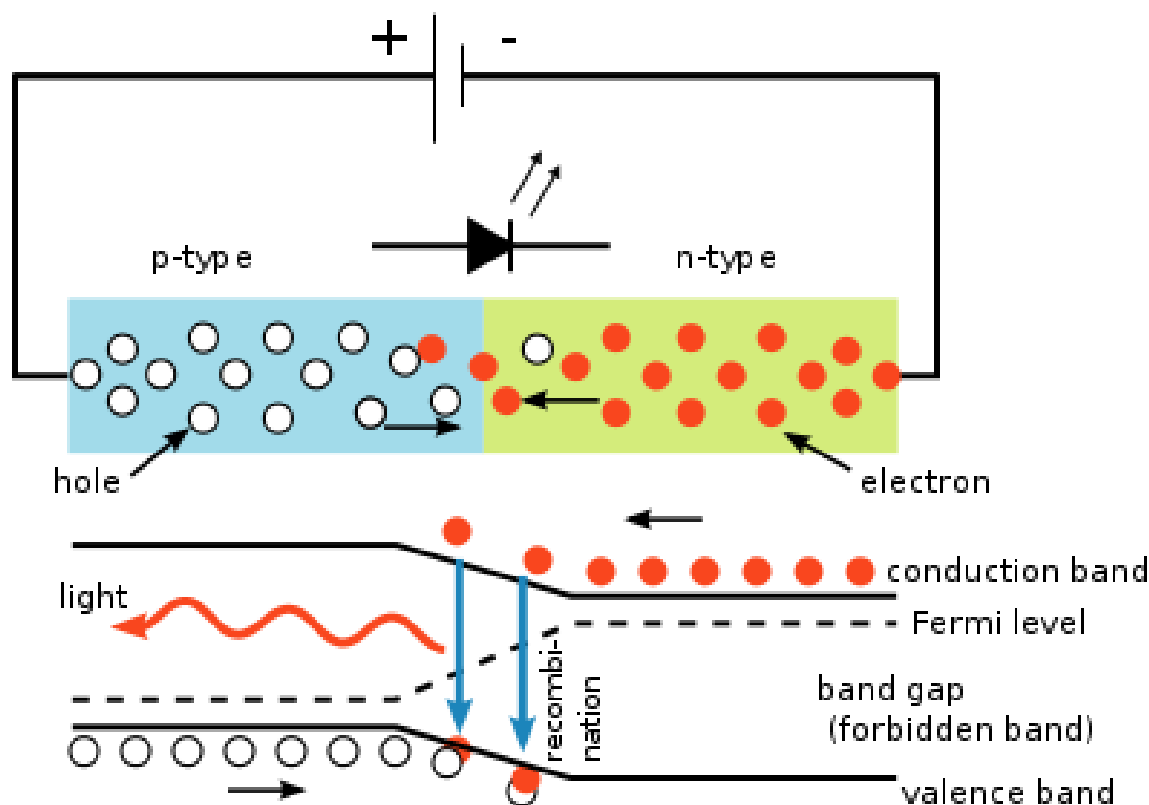
# Semiconductor Diode

- Semiconductors can be P and N type
- The junction between P and N type silicon forms an energy barrier and creates a diode


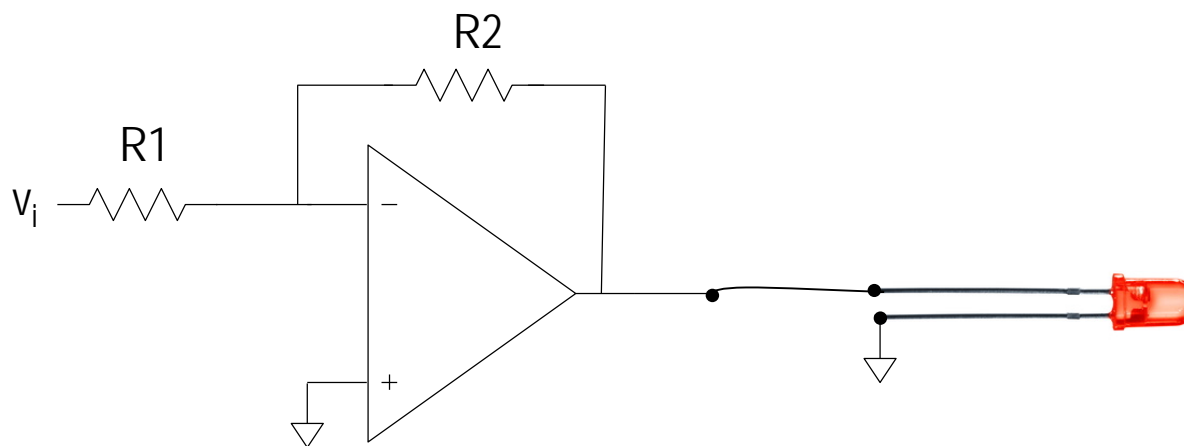
# Diodes and LEDs


- We don't need to model all of the detailed physics to use diodes
- Just choose the modeling abstraction that is required for our design



- ▼ We have a model for the opamp
- ▼ Choose a model for the nonlinear LED based on how much precision we need
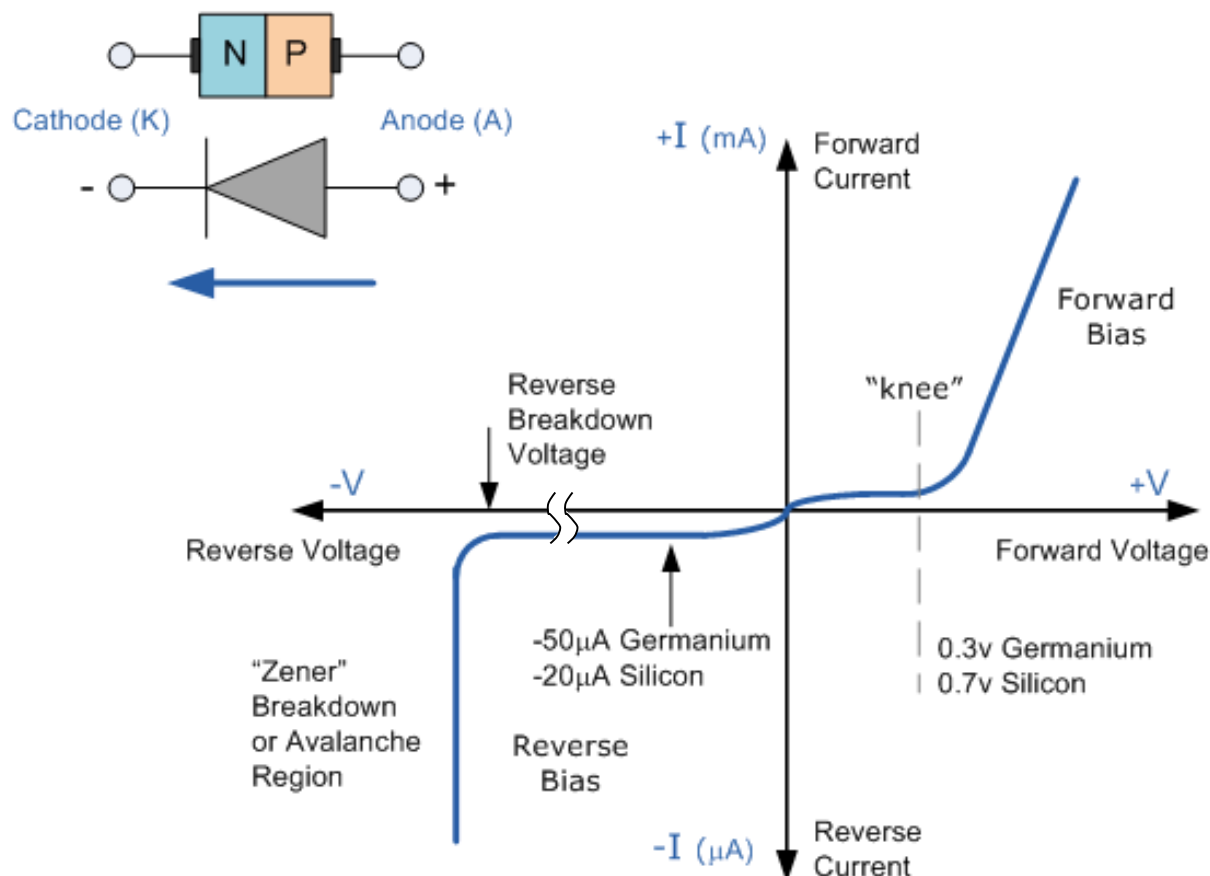
# Diode Models

- Diodes are characterized by *nonlinear* behavior
- LEDs have the same I-V characteristic, but a diode model does not capture the photon emissions




# Diode Models

- Current-voltage relationship follows an *exponential* behavior in the *forward* bias range

$$i_D = I_S \left( e^{v_D/V_T} - 1 \right) \quad \text{Diode eqn}$$

Forward current region
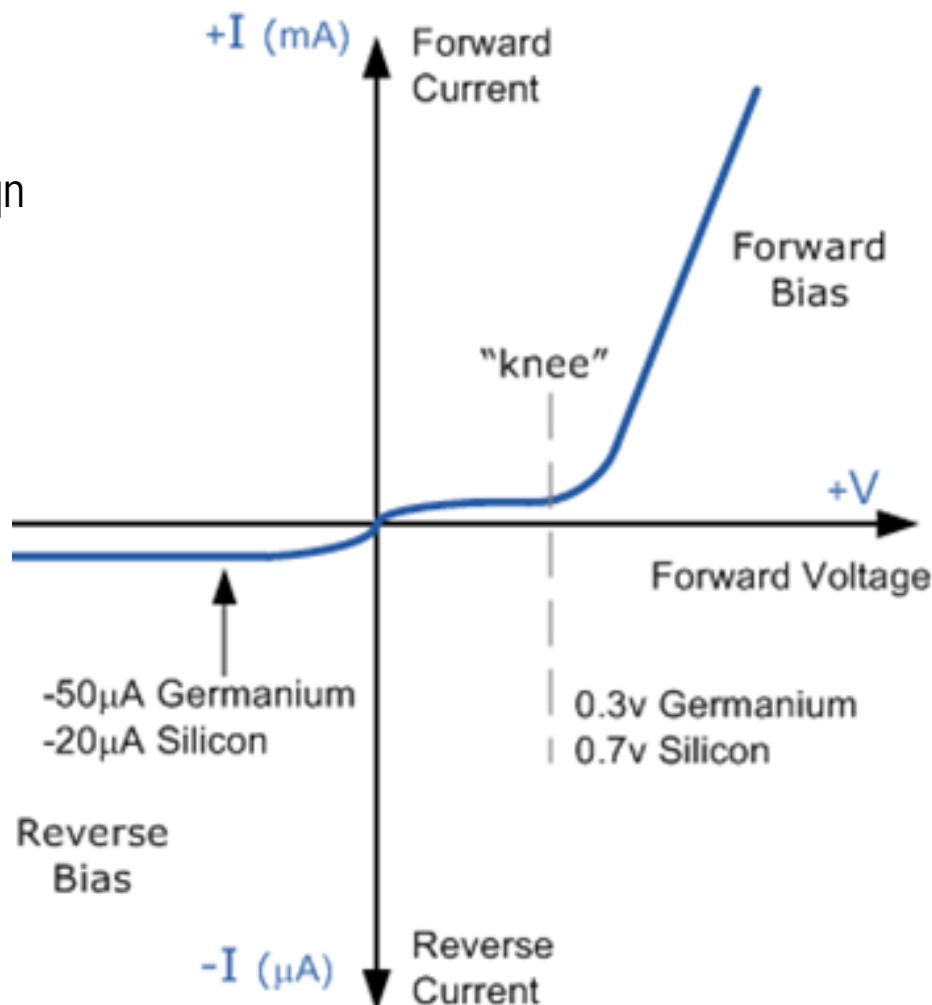
$$i_D \approx I_S e^{v_D/V_T} \quad v_D > 0$$



# Terminology Difference


- Note that I am representing the thermal voltage as  $V_T$
- The book refers to it as  $V_{TH}$

$$i_D = I_S \left( e^{v_D/V_T} - 1 \right) \qquad V_T = \frac{KT}{q}$$

- Relationship between current and potential voltage across a p-n junction depends on the thermal voltage
  - ▼  $q$  is the charge on the electron –  $1.602 \times 10^{-19}$  C
  - ▼  $k$  is Boltzmann's constant –  $1.3806 \times 10^{-23}$  J/K
  - ▼ At room temperature ( $\approx 300$  K) the thermal voltage is  $\sim 26$  mV
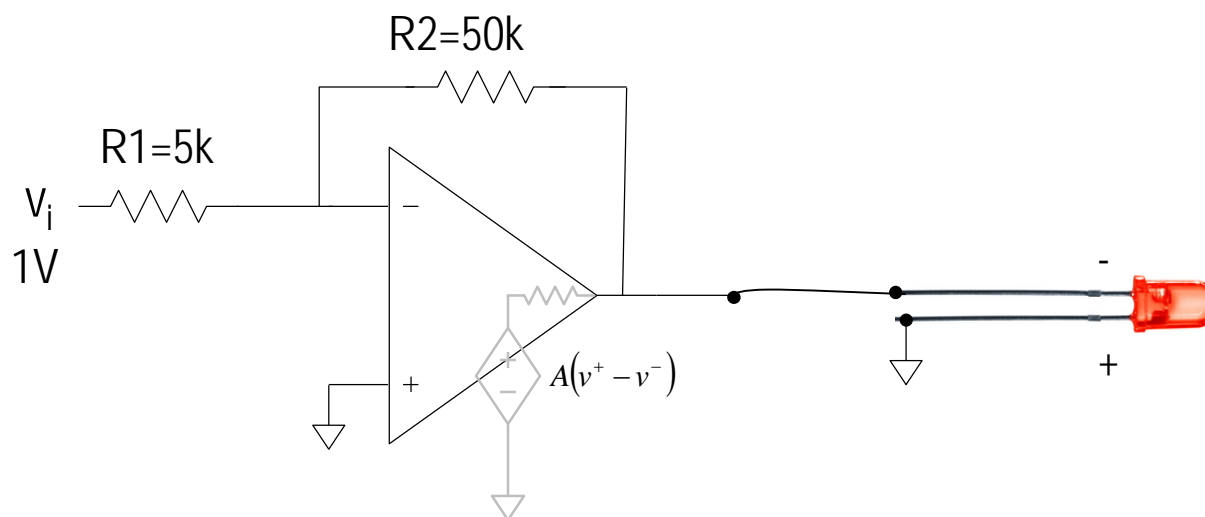
# Diodes and LEDs

- If the opamp **output resistance** is really small, there is nothing to limit the diode current and voltage
- What would happen to it?




- For the nonideal opamp,  $v^-$  becomes whatever value it needs to be so that

$$-Av^- \approx 10v_i$$



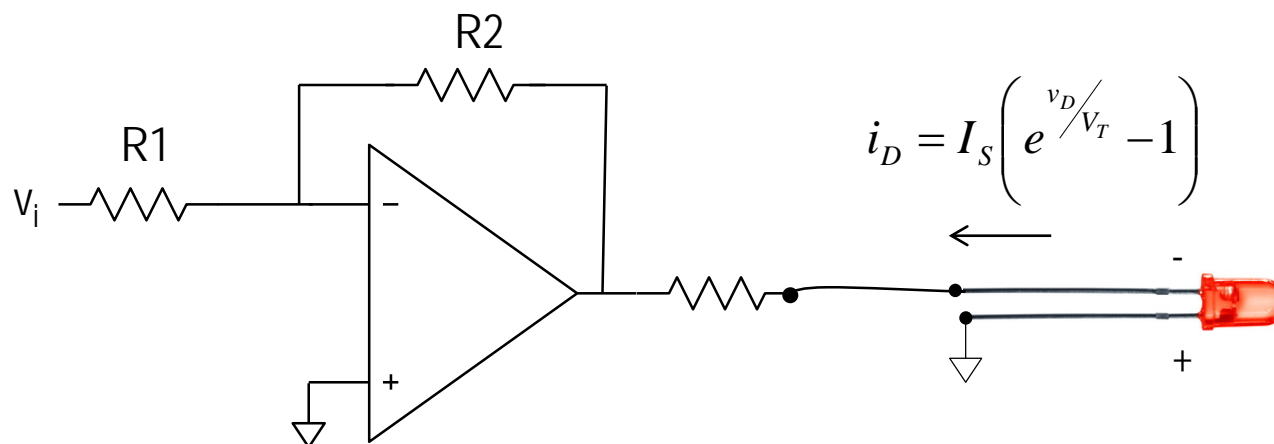
# Limiting Current

- In the lab we would want to add a series resistor to limit the current



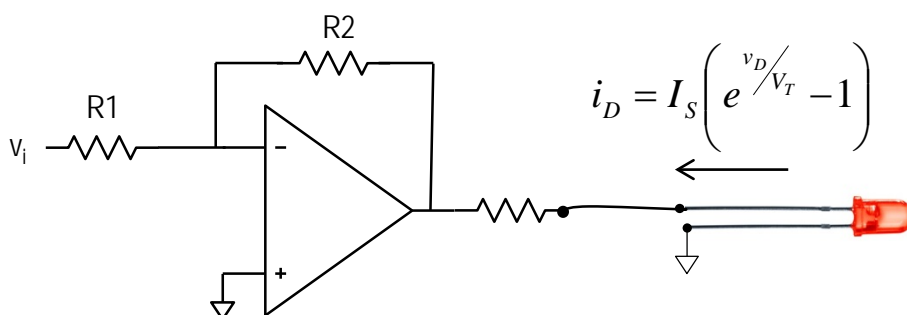
# Engineering Approximations

- Can approximate the diode voltage as the “knee” voltage




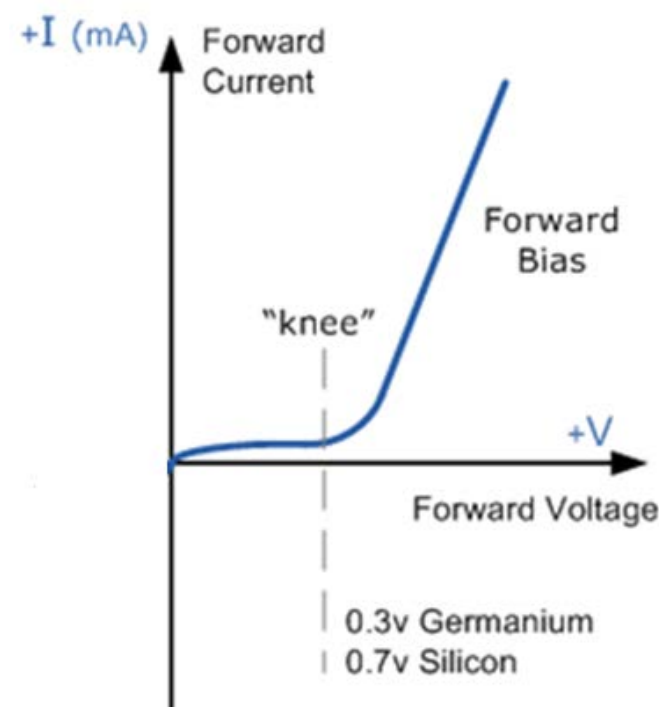
$$i_D = I_S \left( e^{v_D/V_T} - 1 \right)$$



- NOTE: the value of the knee voltage depends on the *current range* for which you are using the diode

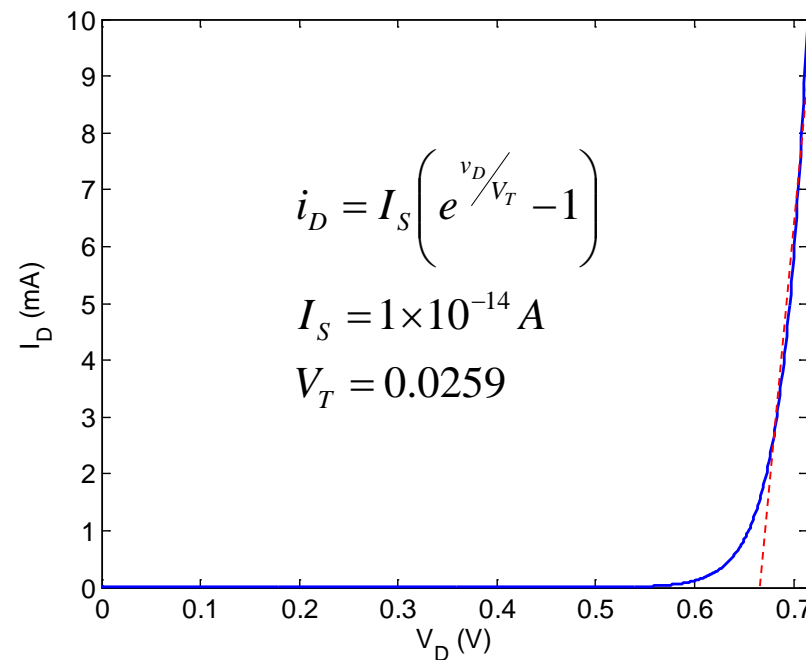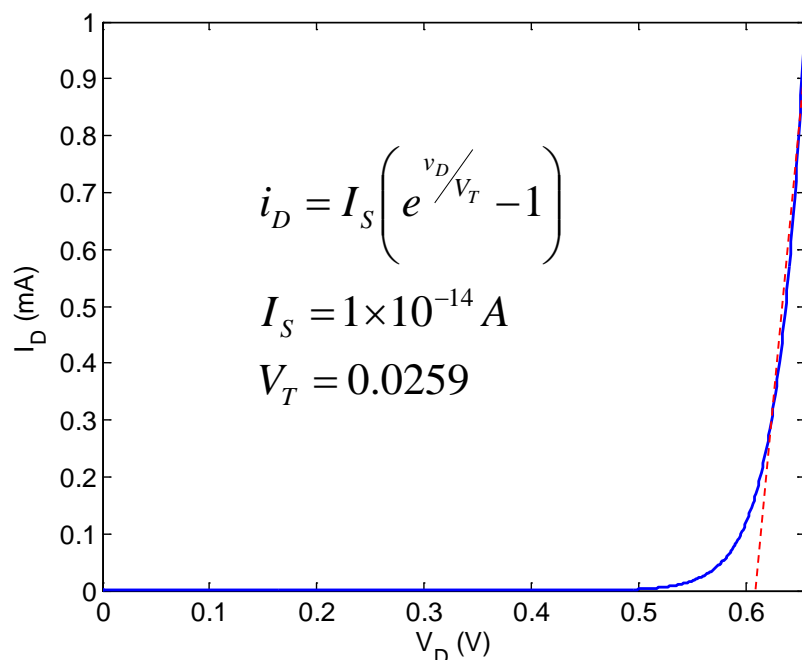
# "Knee Voltage" or "On Voltage"

- Exponential function looks like the same shape when plotted over any current range
- Changing diode plot to cover a larger current range corresponds to a larger "knee voltage"




# Engineering Approximations

## ■ How do we solve nonlinear circuits?

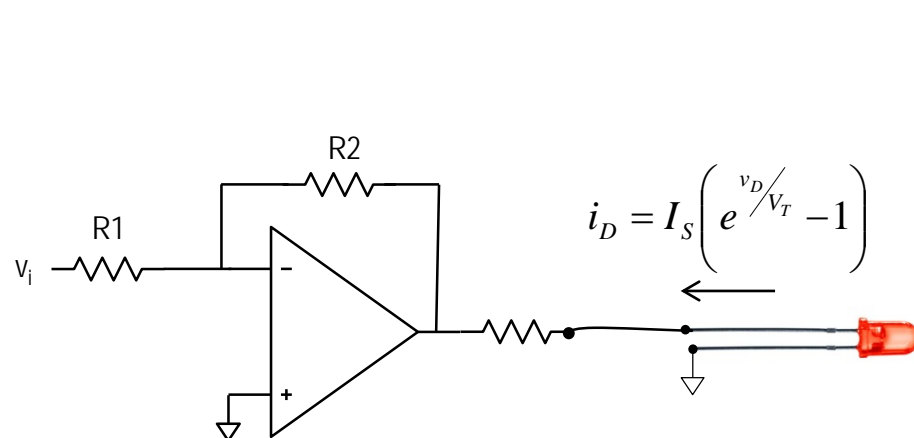
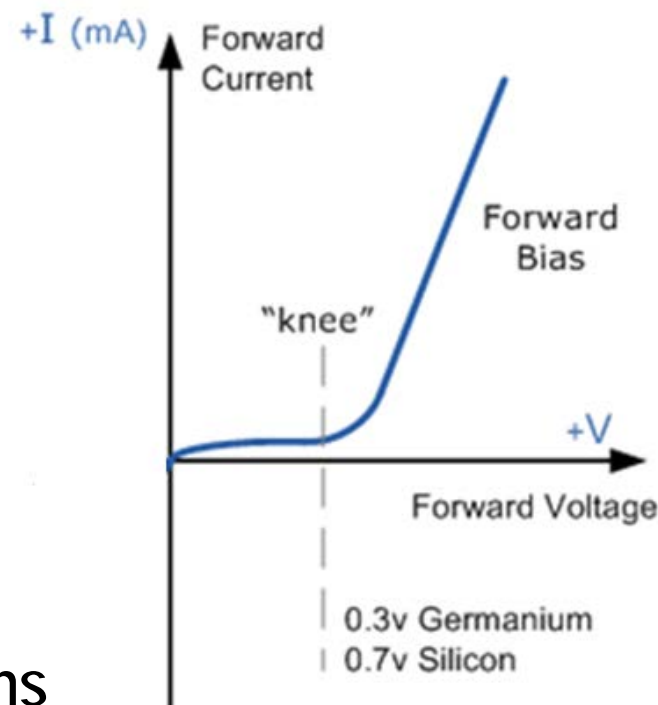
$$i_D = I_S \left( e^{v_D/V_T} - 1 \right)$$




## ■ Do we need to solve nonlinear equations for what we are trying to do?

- ▼ Iterative solutions can be done as via Newton Method, etc.
- ▼ Is our model precise enough to warrant that?
- ▼ Does our design require such precision?

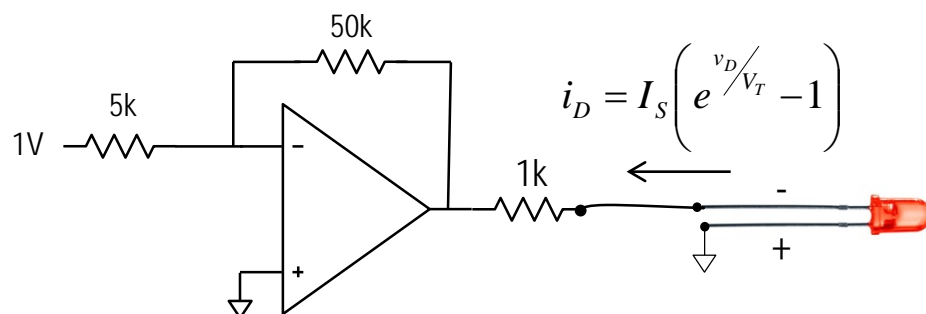
# Engineering Approximations

- For our simple LED driver, does our design change significantly if the diode voltage is 0.6 or 0.7 volts?


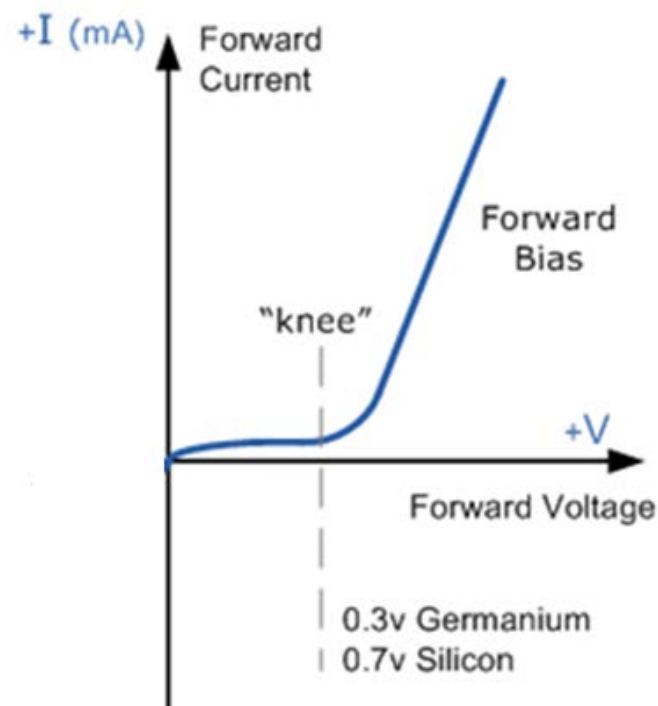
## EXERCISE:


- Assume knee voltage is 0.7V, and solve for current
- Next do the same with a knee voltage of 0.6V and compare the values


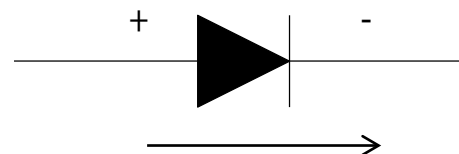
# Diode Model

- All diode models follow reference directions for current and voltage


$$i_D = I_S \left( e^{v_D/V_T} - 1 \right)$$



- They are *passive elements* that can only *dissipate or absorb power*
  - ▼ Voltage direction establishes current direction
- For an LED, the illumination intensity is proportional to  $I$
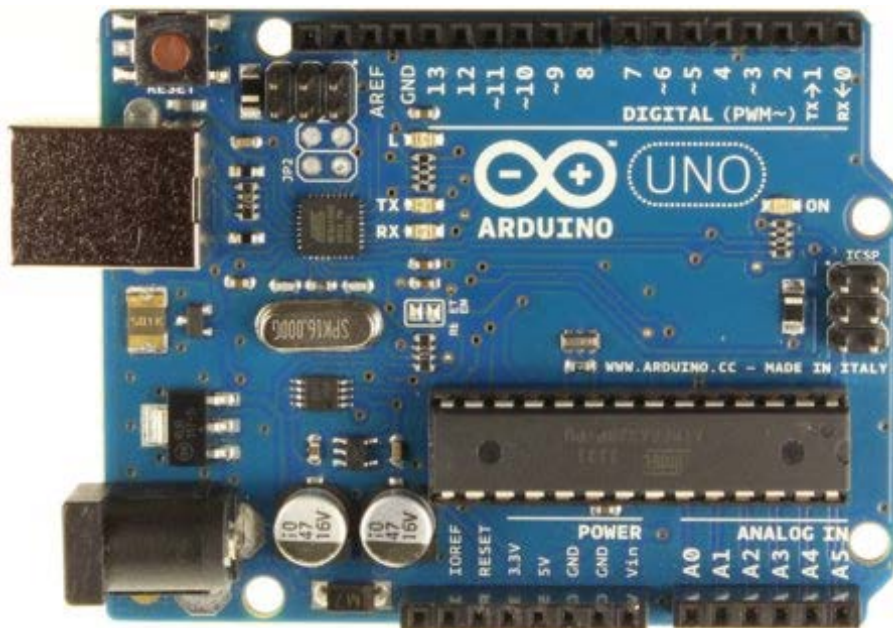
# Diodes

- In Lab 1 you will use an Arduino board and an IR diode to build a TV ~~remote~~ <sup>remote</sup> controller



IR diode

# Infrared Light

## ■ Visible light


- ▼ Wavelengths from ~390 to 750 nm, or 400–790 THz

## ■ Ultraviolet (UV) light

- ▼ Electromagnetic radiation with a wavelength shorter than that of visible light
- ▼ 10 nm to 400 nm, 790 THz - 30 PHz
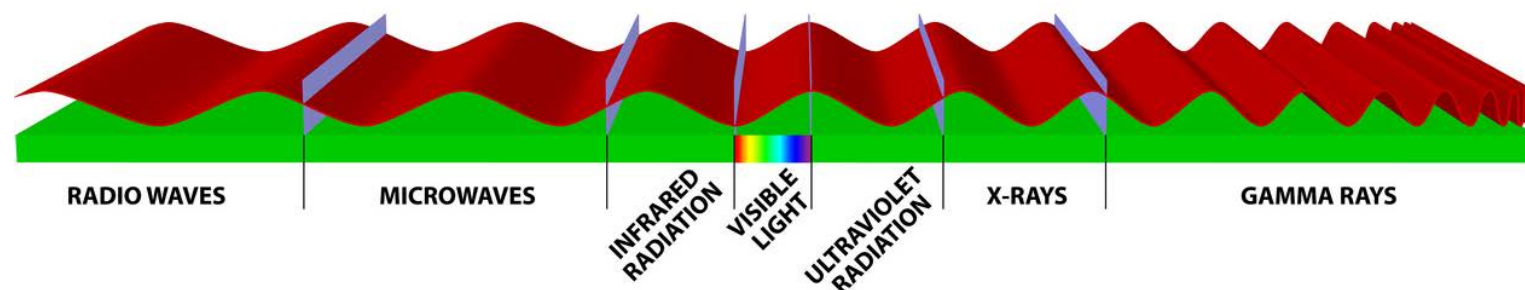
## ■ Infrared (IR) light


- ▼ Electromagnetic radiation with longer wavelengths than those of visible light
- ▼ From the edge of the visible spectrum at 740 nm to 1 mm
- ▼ ~300 GHz - 400 THz, and includes thermal radiation
- ▼ Emitted or absorbed by molecules when they change their rotational-vibrational movements





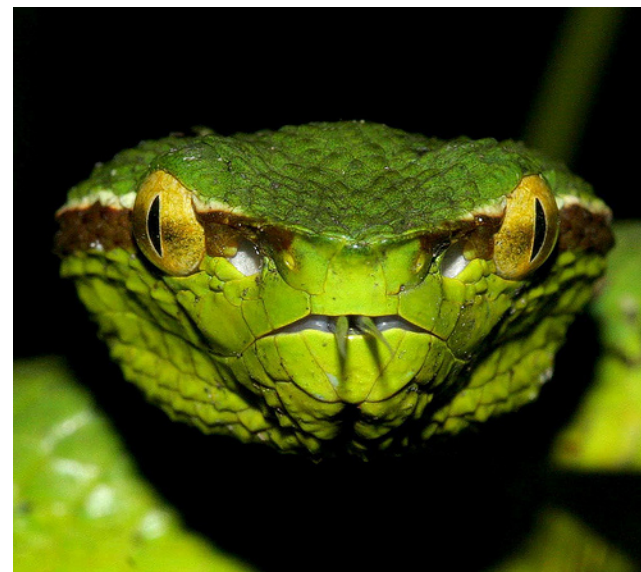
# IR Light

- Human eyes have evolved to filter colors to see red, green and blue
  - ▼ Needed to recognize danger (poisonous plants), or human emotions (blushing), etc.
- Humans cannot see IR light due to our filtering, but we use IR cameras to see in the dark
- Some animals have adapted to be more sensitive to IR light
  - ▼ Pit vipers use it to detect warm bodies of prey
  - ▼ Some insects, such as moths and mosquitos are drawn to IR light




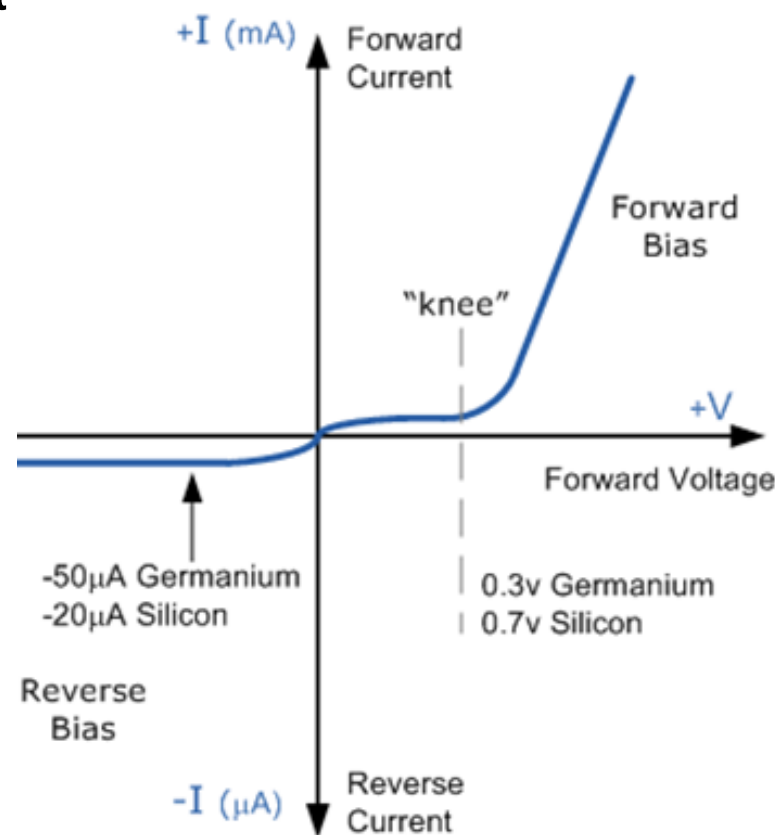
# Photodiodes

- Remote control transmits IR signals, and TV has an IR sensor to receive them
- **Photodiodes** work the same as IR LEDs – but in reverse
- IR diode is reverse-biased so that the electrons are swept out by a strong electric field
- Produces a small, but measurable current that can be converted to a voltage, amplified, filtered, etc.


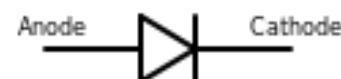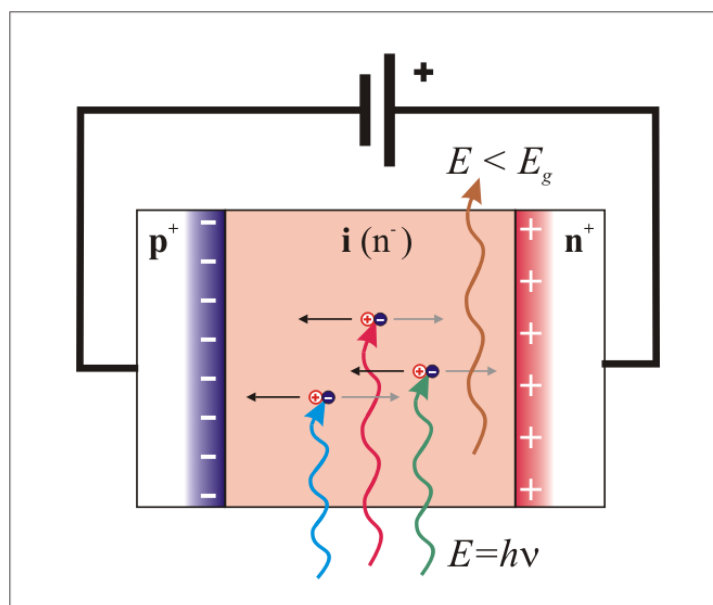
# Photodiodes


- Solar cells are large photodiodes
- Electrons freed when a photon with energy greater than or equal to bandgap strikes the photodiode
- PIN diode has an intrinsic lightly doped inner layer where light energy excites an electron and creates a free electron



- You'll use photodiodes in some of the lab assignments


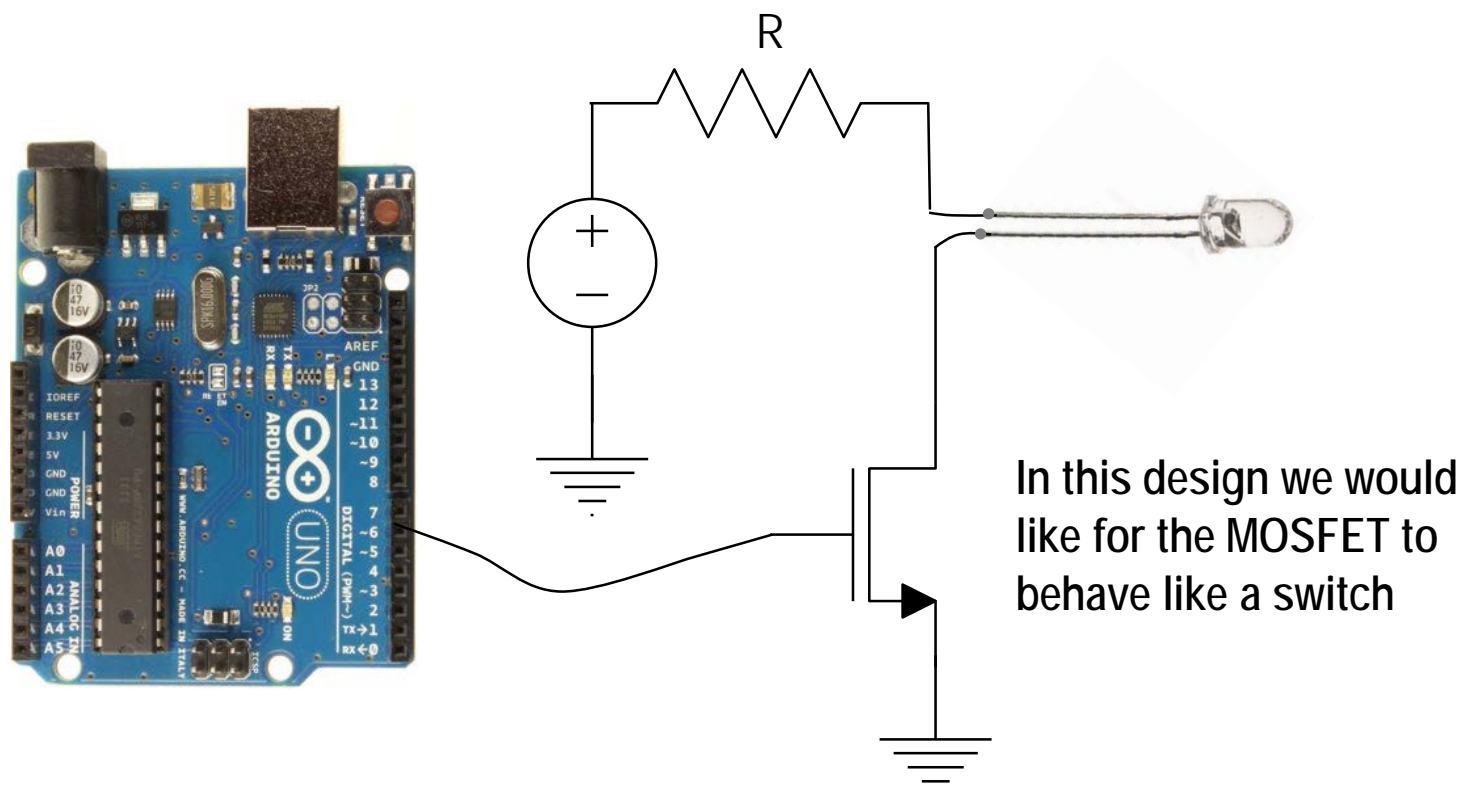
# Lab 1

- Output drivers on Arduino provide limited current
- You are going to use MOSFETs to drive more current through the IR diode for longer range



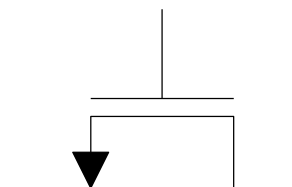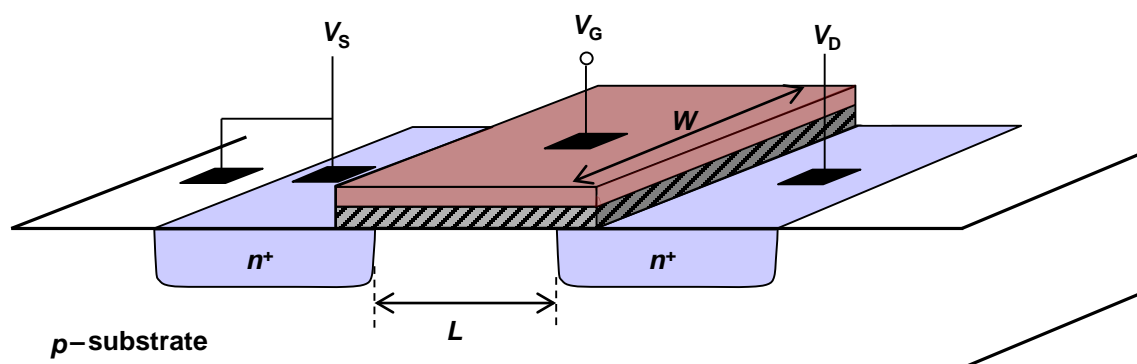
# MOSFETs

- Transistors are more complex nonlinear models than diodes
- Three terminal MOSFETs are often used *when the substrate is connected to the source*





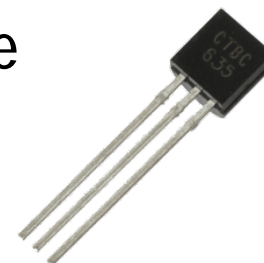- Discrete transistor parts generally have source connected to bulk


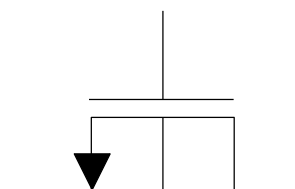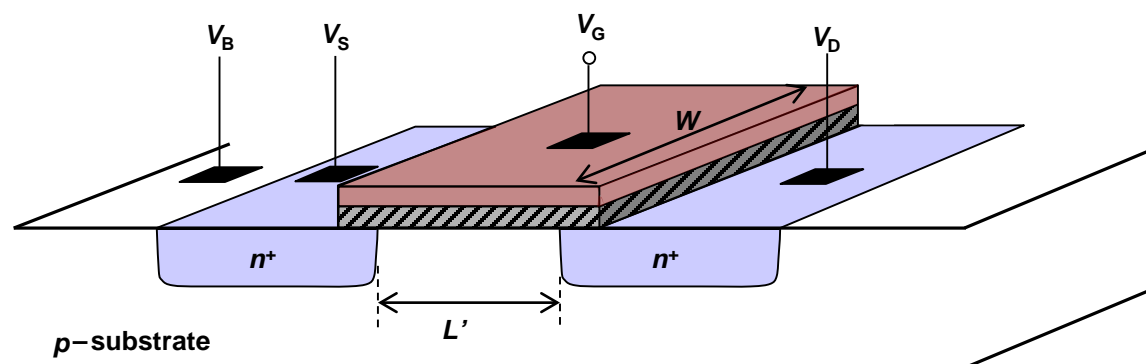
# Nonlinear Models


- But bulk substrate MOSFETs introduce a 4-th node in general



- Most integrated circuit transistors require you to properly configure all four terminals
- But modern Silicon on Insulator (SOI) transistors on an IC have no body connection since the substrate is a floating node

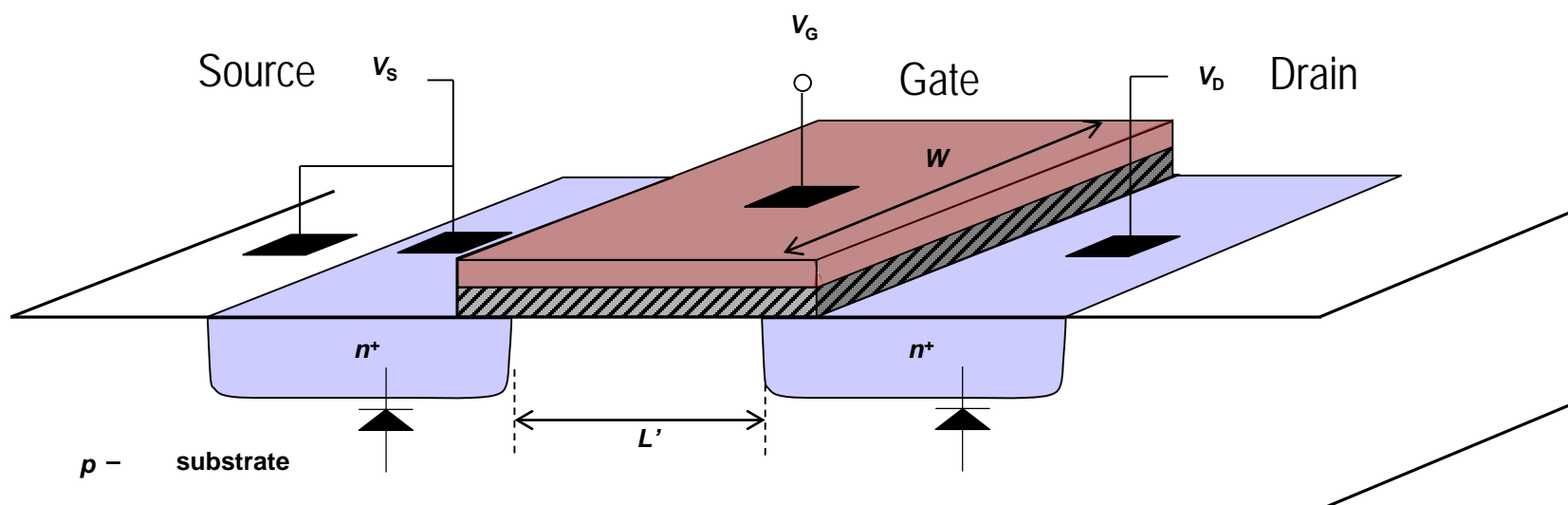
# Brief Overview MOSFET Physics

- p-n junctions form unwanted diodes, so they must be biased to never become forward active (turn “on”)


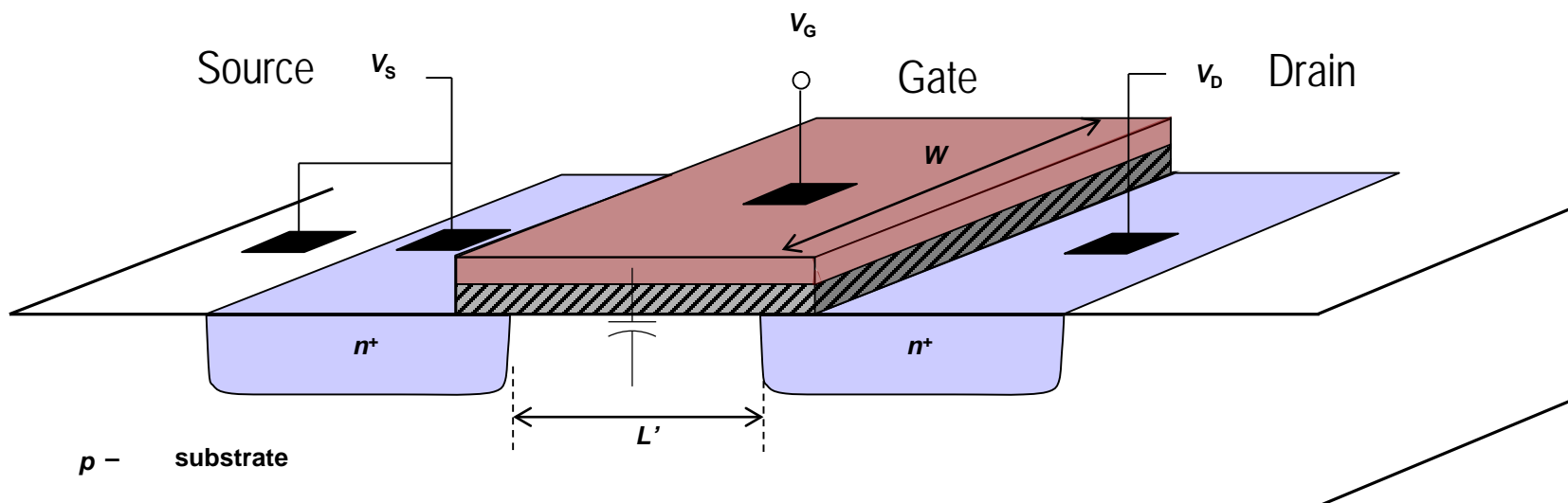
# MOSFETs


- Electrical insulating layer between gate and channel creates a capacitor between gate and channel
- The channel is not an electrical node, but it is connected to the source and drain nodes





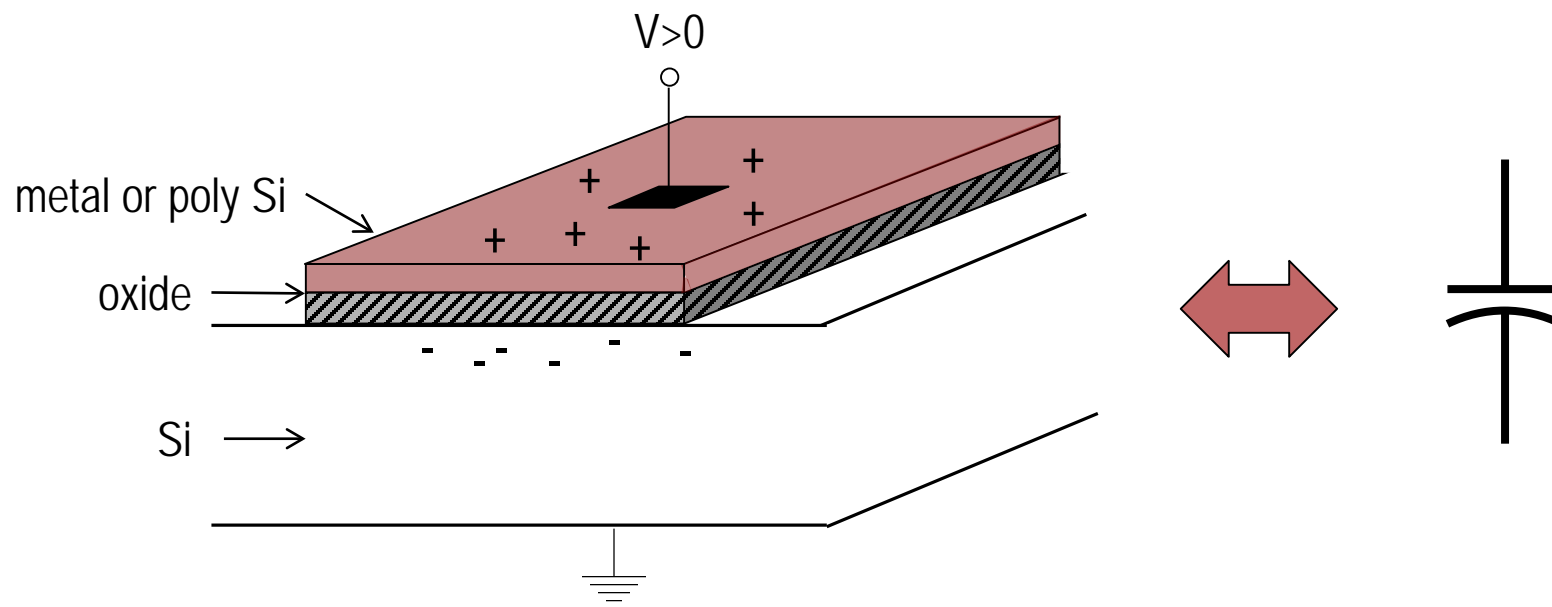
# Capacitance

- Physics II will cover parallel plate capacitance


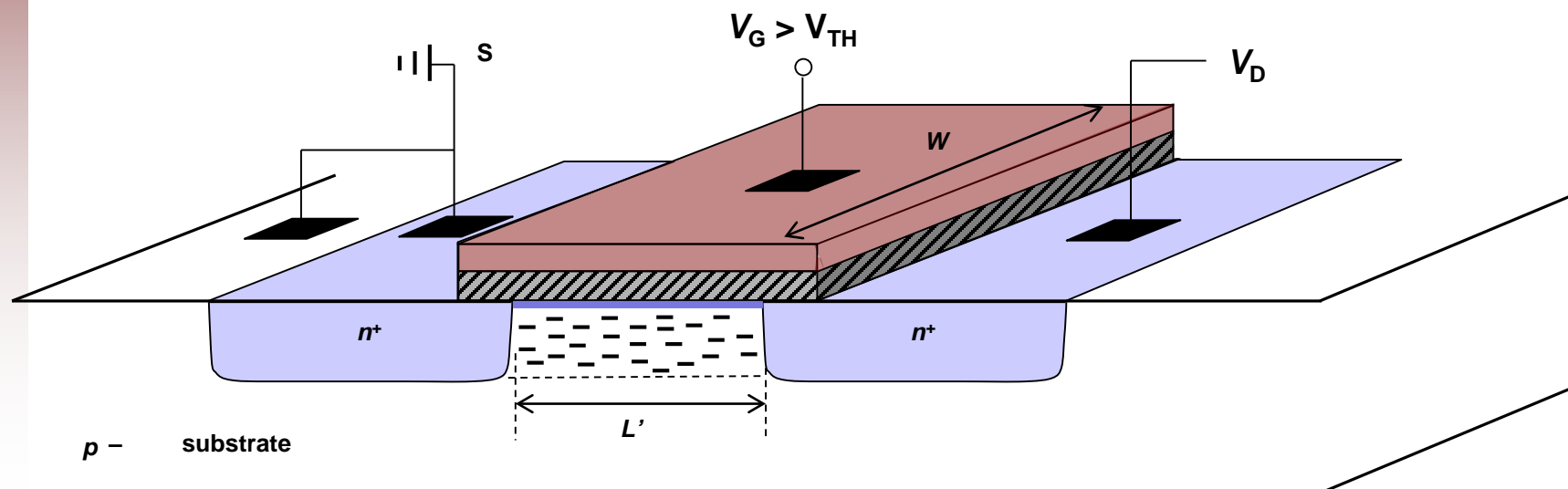
# MOSFETs

- After the gate voltage exceeds the threshold voltage, the negative charge in the channel forms a conducting layer



- Current now flows from drain (higher voltage) to source
- Or, electrons flow from source and end up in drain
- Channel forms a resistance between drain and source




# MOSFET Abstraction

$I_D \cong 0$  cutoff :  $V_{GS} < V_{TH}$  Subthreshold (leakage) current

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2 \quad \text{saturation : } V_{DS} > V_{GS} - V_{TH}$$




$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \quad \text{triode : } V_{DS} < V_{GS} - V_{TH}$$

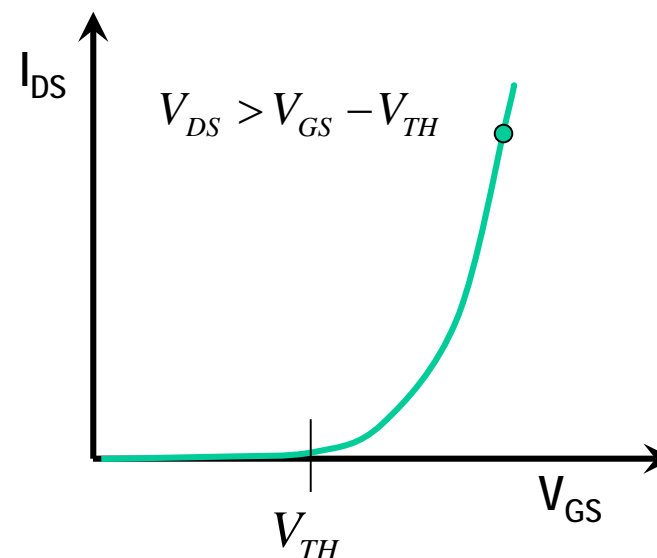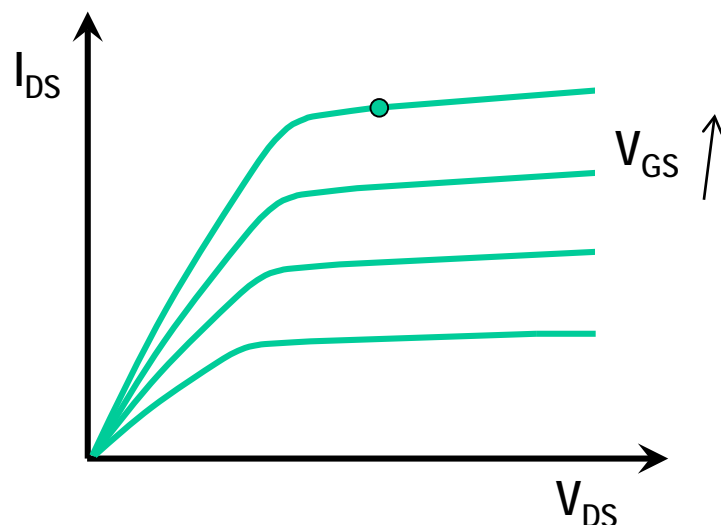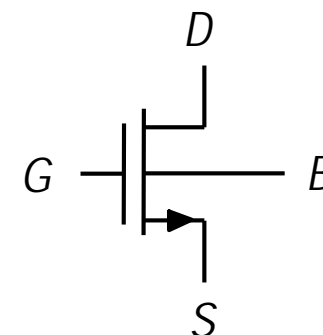where  $V_{TH} = V_{TH0} + \gamma (\sqrt{2\phi_F - V_{BS}} - \sqrt{2\phi_F})$


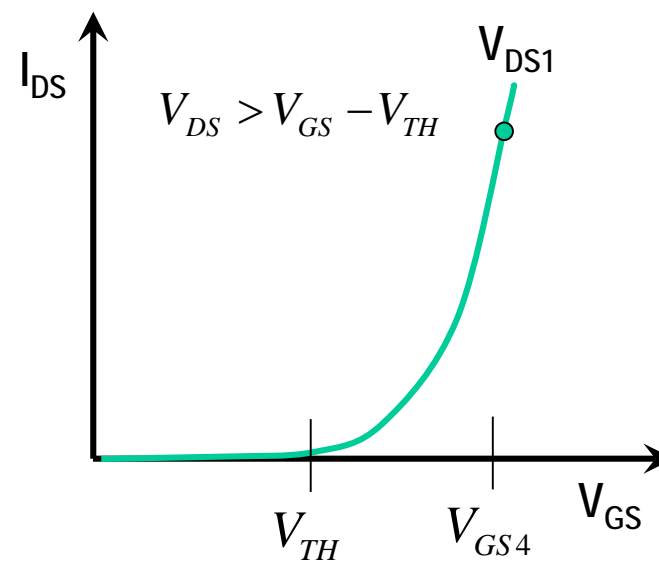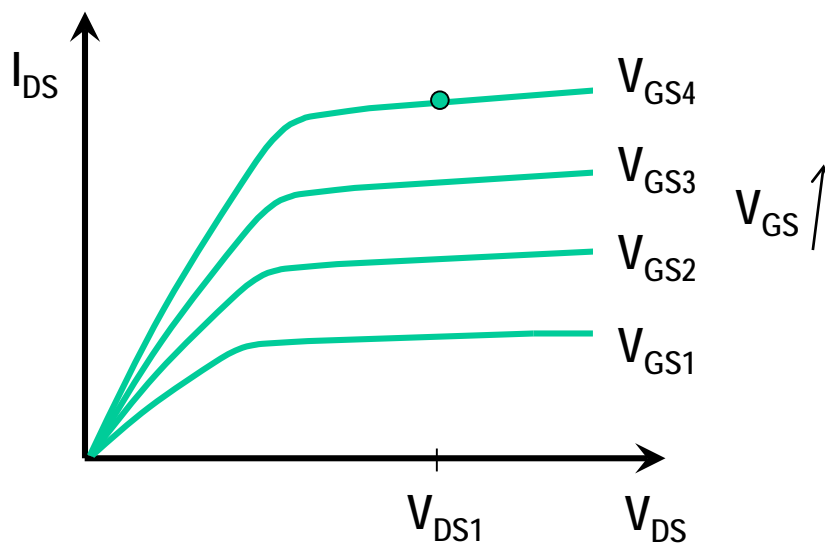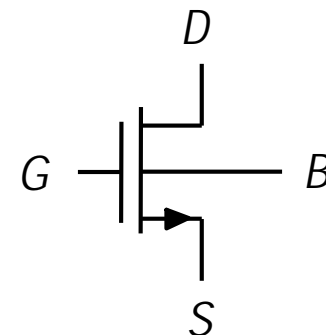
# MOSFET Voltages


- Note that voltages are *between* two nodes
- Gate voltage (relative to the source) controls the current flow in the channel (turns on/off)
- Source and Drain nodes are defined by voltages
- MOSFET turns “on” when  $V_{GS}$  exceeds **threshold voltage**


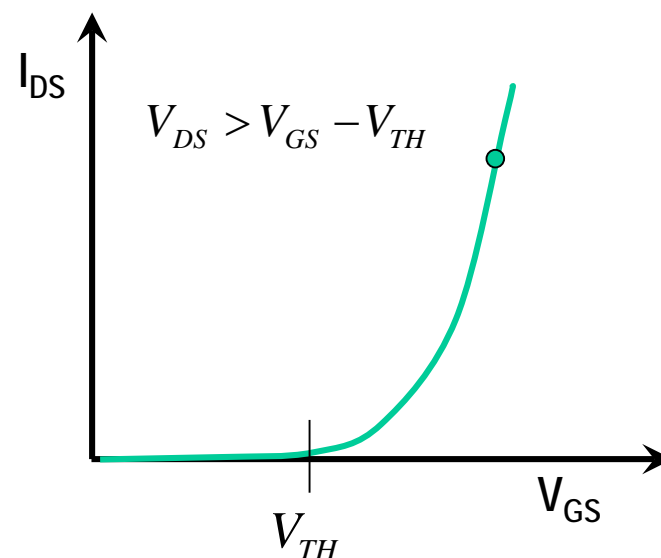
# Terminology Difference

- Note that I am representing the threshold voltage as  $V_{TH}$
- The book refers to it as  $V_T$

- It represents the gate-to-source voltage for which the channel becomes strongly conducting





# MOSFET Equations

- MOSFET channel is a nonlinear resistance

$$V_{DS} < V_{GS} - V_{TH}$$

$$I_D = \frac{K}{2} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$K = \mu_n C_{ox} \frac{W}{L'}$$

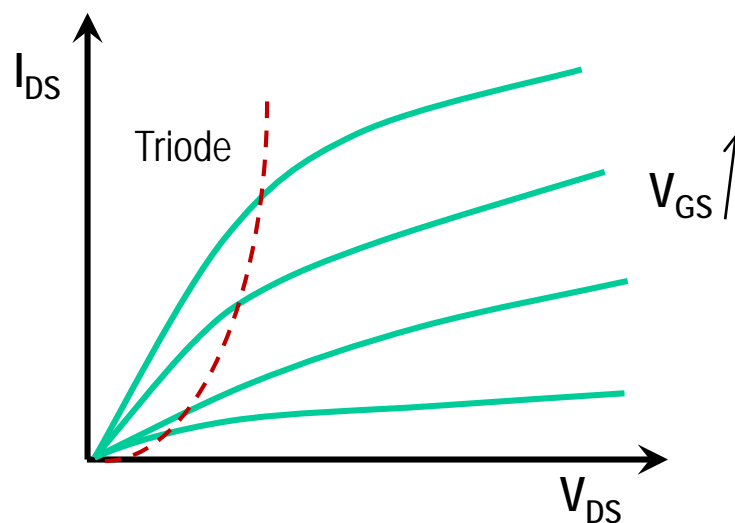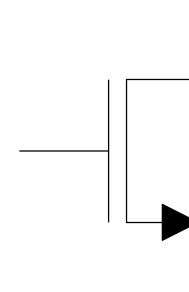


# Linear or Triode Region of Operation

- For small drain to source voltage the MOSFET channel behaves like a voltage controlled resistor

Triode or linear region:
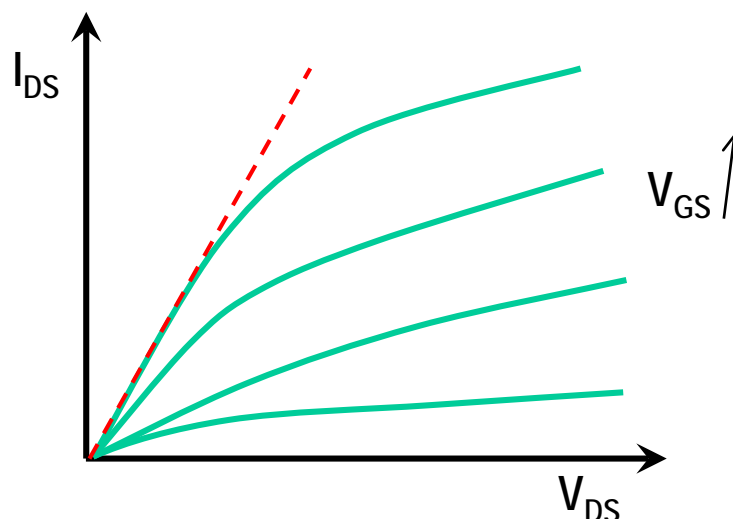
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} [2(V_{GS} - V_{TH})] \cdot V_{DS}$$





# MOSFET Equations

- For small  $V_{DS}$  the controlled resistance is almost linear


$$V_{DS} < V_{GS} - V_{TH}$$

$$I_D = \frac{K}{2} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$K = \mu_n C_{ox} \frac{W}{L'}$$

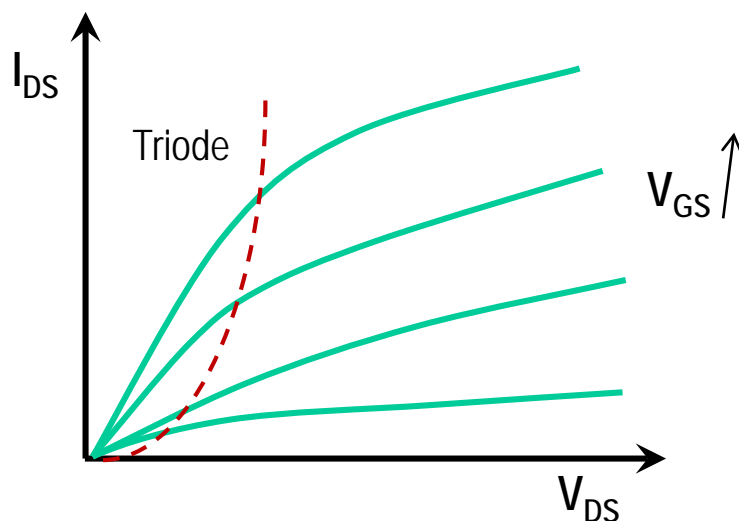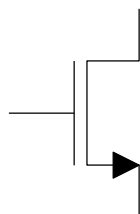


$$G \approx fct(V_{GS})$$

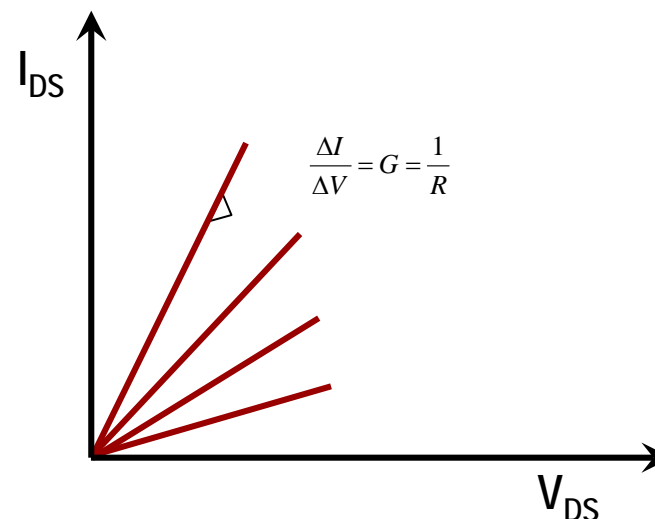



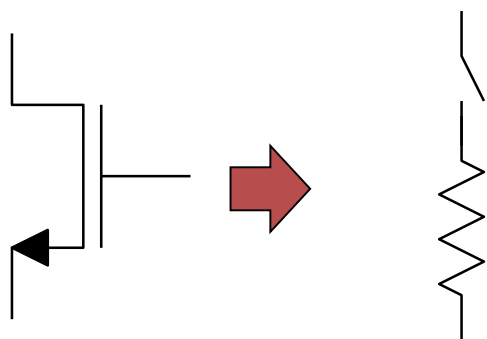
# MOSFET Switches

- For digital applications we often model the transistor as a switch
- But it only behaves like a switched resistance if the drain-to-source voltage is very small



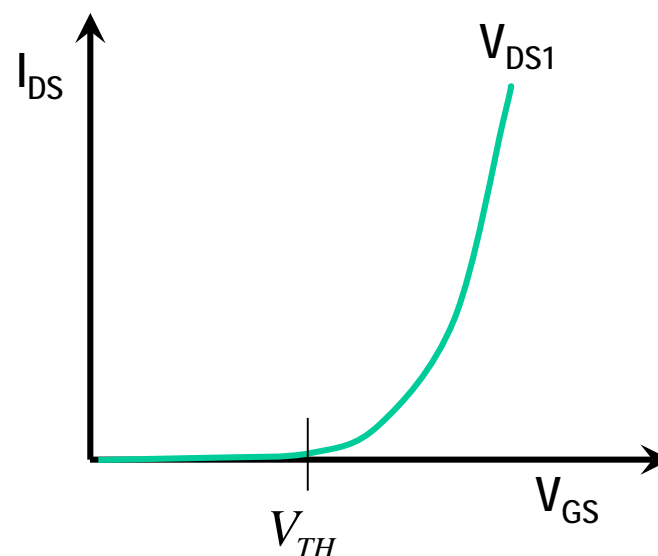$I_D \cong 0$  cutoff for  $V_{GS} < V_{TH}$





# MOSFET Saturation

- The current *saturates* at a maximum value for each value of gate voltage
- MOSFET now behaves like a voltage-controlled current source

Saturation region:

$$V_{DS} > V_{GS} - V_{TH}$$
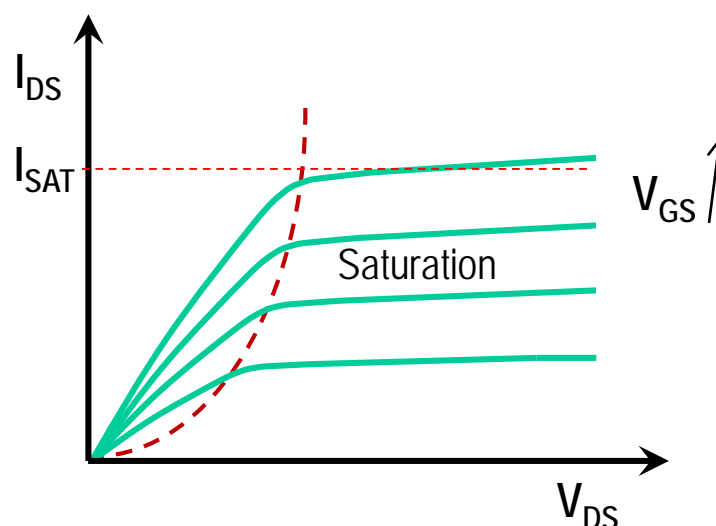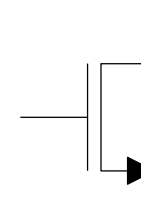
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$




# Take Aways from this Video

- Know the difference between a linear and a nonlinear circuit element
  - ▼ Be able to provide examples of nonlinear elements
- Understand the basics of diodes and LEDs
  - ▼ Diode equation
  - ▼ Does it deliver or dissipate power?
- Appreciate the fundamental operation of a MOSFET
  - ▼ Eventually you'll more fully understand the equations and how to use them
- Recognize a resistance switch model
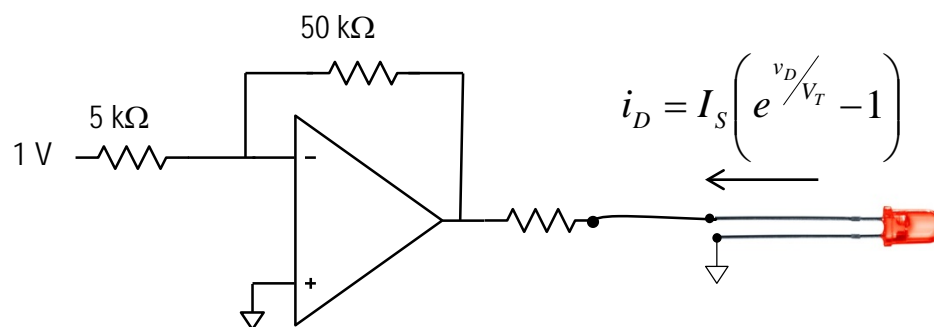
# Example Problem

- What is the current through the diode assuming a 0.7 V drop?
- Is 0.7 V across the diode a good approximation?



# Example Problem

- What is the current through the diode assuming a 0.7 V drop?
- Is 0.7 V across the diode a good approximation?

